

U.G. 4th Semester Examination - 2022

PHYSICS

[HONOURS]

Course Code : PHY-H-CC-T-10

(Analog Systems and Applications Theory)

Full Marks : 40

Time : $2\frac{1}{2}$ Hours*The figures in the right-hand margin indicate marks.**Candidates are required to give their answers in their own words as far as practicable.*

GROUP-A

1. Answer any **five** questions: $2 \times 5 = 10$
- “The barrier potential across a p-n junction diode cannot be measured by placing a voltmeter across the diode terminals.” – Explain.
 - Explain the phenomenon punch through in a transistor.
 - A certain Colpitts oscillator uses a tank circuit with $L=20$ mH, $C_1=200$ pF and $C_2 = 100$ pF. What is the frequency of the oscillation?
 - Calculate β of a transistor for which $\alpha = 0.96$. If α changes by 0.1 %, what is the percent change in β ?

- Show how a logarithmic amplifier can be built with an OP-AMP.
- Why are CC and CB amplifiers not suitable for cascading?
- What is the desired position of the Q-point for a minimum distortion and why?
- In a Zener diode regulator the series resistance is 25Ω Zener voltage 15 V and load resistance 100Ω . The input voltage varies from 20 to 30V. Calculate the minimum and maximum current in the Zener diode.

2. Answer any **two** questions: $5 \times 2 = 10$
- “Negative feedback reduces the gain of an amplifier still this type of feedback is widely used.” Why? The open loop gain of an amplifier changes by 6%. If 10 dB negative feedback is applied, calculate the percentage change of the closed loop gain. $2+3$
 - What is self bias? Draw the circuit diagram showing the self bias of an NPN transistor in the CE configuration. Explain physically how the self biasing resistor improves the stability. $1+2+2$

c) Why are junction transistors called bipolar devices? What is early effect? With respect to CB output characteristics of a transistor explain the active saturation and cutoff regions.

1+1+3

d) State the different methods of coupling of amplifiers. Give a brief account of class A, B, AB and C amplifiers.

2+3

3. Answer any **two** questions: 10×2=20

a) Discuss the mechanism of amplification obtained in a transistor. What is the origin of the name ‘transistor’? Draw a neat circuit diagram of an emitter follower. A transistor having $\alpha = 0.97$ and a reverse saturation current $I_{CO} = 13 \mu A$, is operated in CE configuration. What is β for this configuration? If the base current is $240 \mu A$, calculate the emitter current and the collector current.

3+1+2+4

b) What are the advantages of using h-parameters (two port representation of transistor) model? Draw the small signal low frequency hybrid parameter equivalent circuit of a CE amplifier and derive expression for current gain, voltage gain, input impedance and output impedance.

A transistor amplifier in CE configuration couples a source of internal resistance $2 k\Omega$ to a load of $20 k\Omega$. Find the input and the output resistances if $h_{ie} = 1$.

1+(2+4)+3

c) Explain the virtual ground concept in OP-AMP with a diagram. Show how an OP-AMP can be used as summing amplifier, subtractor and integrator. Calculate the actual output voltage of an integrator after 2 seconds for the input voltage of 1 V d.c. Given that input resistance equal to $200 k\Omega$ and feedback capacitance $1 \mu F$.

2+(2+2+2)+2

d) What is a D/A converter? Explain the principle of operation of a weighted-resistor D/A converter. What is its disadvantage and how is it removed in a ladder converter? In a 4-bit weighted resistor D/A converter the resistor value corresponding to LSB is $16 k\Omega$. Find the resistor value corresponding to MSB.

1+3+(1+3)+2
